1

Navrhněte Mealyho automat pro realizaci a ovládání a signalizace výtahu. Budova má 0 - 3 pater. Výtah se pohybuje pomocí tlačítek pater 0 - 3 a motoru. Na výstupu signalizujte pohyb nahoru nebo dolů (L4, L5) a o kolik pater se posune (L0 o 1 patro, L1 o 2 patra a L3 o 3 patra). Aktuální patro je zobrazeno na sedmisegmentu. Pokud výtah stojí svítí všechny 3 Ledky (L0,L1,L2).

2.

Spartan

Spartan je lehká vývojová deska FGA, je založenqa na řipu Xilinx Spartan-7 Můžete použít s Arduinem k ovládání LCD a fotoaparátu nebo jako samostatnou vývojovou desku FPGA.

Místo makrobuňek obsahují logické bloky Log. Bloky jsou navzájem propojeny globální propojovací maticí

Obsahuje SRAM

VHDL

Používá se pro návrh a simulaci digitálních integrovaných obvodů, například programovatelných hradlových polí (CPLD,FPGA) nebo různých zákaznických obvodů(ASIC)

Jazyk VHDL může být požit i jako paralelní programovací jazyk.

3.

Vstupní stavy						
	btn3	btn2	btn1	btn0		
x4	0	0	0	0		
x0	0	0	0	1		
x1	0	0	1	0		
x2	0	1	0	0		
x3	1	0	0	0		


			_
Vnitřní stavy			
	Q1	Q0	
s0	0	0	0 Patro
s1	0	1	1 Patro
s2	1	0	2 Patro
s3	1	1	3 Patro

Výstupní stavy							
	L5	L4	L3	L2	L1	LO	
y0	0	0	0	1	1	1	
y1	0	1	0	0	0	1	Nahoru o 1 patro
y2	0	1	0	0	1	0	Nahoru o 2 patra
у3	0	1	0	1	0	0	Nahoru o 3 patra
y4	1	0	0	0	0	1	Dolu o 1 patro
y5	1	0	0	0	1	0	Dolu o 2 patra
у6	1	0	0	1	0	0	Dolu o 3 patra

y= f(S) Moore... Závislý na vnitřním stavu

y= f(X,S) Mealy... Závislý na vnitřním stavu a vstupu

5.

 

6.

	x0	x1	x2	х3	у
S0	s0	s1	s2	s3	y0 - y3
s1	s0	s1	s2	s3	y0 - y2, y4
s2	s0	s1	s2	s3	y0 - y1,y4 -y5
s3	s0	s1	s2	s3	y0, y4 - y6

DEKODER

```
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
entity dekoder is
    Port ( stavy : in STD LOGIC VECTOR (1 downto 0);
          LED : out STD LOGIC VECTOR (6 downto 0));
end dekoder;
architecture Behavioral of dekoder is
begin
with stavy select
  LED<= "1111001" when "01", --1
    "0100100" when "10", --2
    "0110000" when "11", --3
    "1000000" when others; --0
end Behavioral;
```

DELICKA

```
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD LOGIC UNSIGNED.ALL;
entity delicka is
    Port ( CLK_in : in STD_LOGIC;
          CLK out : out STD LOGIC);
end delicka;
architecture Behavioral of delicka is
begin
   process (CLK in)
      variable i : integer range 0 to 15000000;
begin
   if rising_edge(CLK_in) then
     if i=0 then CLK_out <= '1';
             i := 9843000;
      else
             CLK out <= '0';
             i := i - 1;
      end if ;
    end if ;
   end process;
end Behavioral;
```

Hl.program

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity main is
  Port ( clock : in STD_LOGIC;
      reset: in STD_LOGIC;
      kam: in STD_LOGIC_VECTOR (3 downto 0);
     vyst : out STD_LOGIC_VECTOR (5 downto 0);
      patro : inout STD_LOGIC_VECTOR (1 downto 0));
end main;
architecture Behavioral of main is
signal state, next_state : std_logic_vector(1 downto 0);
             constant s0 : std_logic_vector(1 downto 0) := "00";
             constant s1 : std_logic_vector(1 downto 0) := "01";
             constant s2 : std_logic_vector(1 downto 0) := "10";
             constant s3 : std_logic_vector(1 downto 0) := "11";
begin
SYNC_PROC: process (clock)
 begin
 if rising_edge (clock)
                        then if (reset='0')
                                   then state <= next_state;
                                   else state <= s0;
                        end if;
             end if;
 end process SYNC_PROC;
 OUTPUT DECODE: process (state, kam)
Begin
case (state) is
             when s0 =>
                        if (kam = "( "000111";
                        elsif (kam = "0010") then vyst <= "010001";
                        elsif (kam = "0100") then vyst <= "010010";
                        elsif (kam = "1000") then vyst <= "010100";
                        else vyst <= "000000";
                        end if;
             when s1 =>
                        if (kam = "( "100001";
                        elsif (kam = "0010") then vyst <= "000111";
```

```
elsif (kam = "0100") then vyst <= "010001";
                        elsif (kam = "1000") then vyst <= "010010";
                        else vyst <= "000000";
                        end if;
             when s2 =>
               if (kam = "100010";
                        elsif (kam = "0010") then vyst <= "100001";
                        elsif (kam = "0100") then vyst <= "000111";
                        elsif (kam = "1000") then vyst <= "010001";
                        else vyst <= "000000";
                        end if;
             when s3 =>
               if (kam = "100100";
                        elsif (kam = "0010") then vyst <= "100010";
                        elsif (kam = "0100") then vyst <= "100001";
                        elsif (kam = "1000") then vyst <= "000111";
                        else vyst <= "000000";
                        end if;
             when others => NULL;
end case;
patro <= state;
end process OUTPUT_DECODE;
NEXT_STATE_DECODE: process (state, kam)
begin
case (state) is
             when s0 =>
                        if (kam = "0001") then next state <= s0; patro <="00";
                        elsif (kam = "0010") then next_state <= s1; patro <="01";
                        elsif (kam = "0100") then next_state <= s2; patro <="10";
                        elsif (kam = "1000") then next_state <= s3; patro <= "11";
             else next_state <= s0;
             end if;
             when s1 =>
             if (kam = "0001") then next_state <= s0; patro <="00";
                        elsif (kam = "0010") then next_state <= s1; patro <="01";
                        elsif (kam = "0100") then next state <= s2; patro <="10";
                        elsif (kam = "1000") then next_state <= s3; patro <="11";
             else next_state <= s1;
             end if;
             when s2 =>
             if (kam = "0001") then next state <= s0; patro <="00";
                        elsif (kam = "0010") then next_state <= s1; patro <="01";
                        elsif (kam = "0100") then next_state <= s2; patro <="10";
                        elsif (kam = "1000") then next state <= s3; patro <="11";
             else next_state <= s2;
```


```
end if;

when s3 =>
    if (kam = "0001") then next_state <= s0; patro <="00";
        elsif (kam = "0010") then next_state <= s1; patro <="01";
        elsif (kam = "0100") then next_state <= s2; patro <="10";
        elsif (kam = "1000") then next_state <= s3; patro <="11";
        else next_state <= s3;
        end if;

when others => NULL;
end case;
patro <= state;

end process NEXT_STATE_DECODE;</pre>
```

end Behavioral;

 

```
# clock pins for Basys2 Board
NET "mclk" LOC = "B8"; # Bank = 0, Signal name = MCLK
# Pin assignment for DispCtl
# Connected to Basys2 onBoard 7seg display
NET "seg<0>" LOC = "L14"; # Bank = 1, Signal name = CA
NET "seg<1>" LOC = "H12"; # Bank = 1, Signal name = CB
NET "seg<2>" LOC = "N14"; # Bank = 1, Signal name = CC
NET "seg<3>" LOC = "N11"; # Bank = 2, Signal name = CD
NET "seg<4>" LOC = "P12"; # Bank = 2, Signal name = CE
NET "seg<5>" LOC = "L13"; # Bank = 1, Signal name = CF
NET "seg<6>" LOC = "M12"; # Bank = 1, Signal name = CG
#NET "dp" LOC = "N13"; # Bank = 1, Signal name = DP
NET "an3" LOC = "K14"; # Bank = 1, Signal name = AN3
NET "an2" LOC = "M13"; # Bank = 1, Signal name = AN2
NET "an1" LOC = "J12"; # Bank = 1, Signal name = AN1
#NET "an0" LOC = "F12"; # Bank = 1, Signal name = AN0
# Pin assignment for LEDs
#NET "Led<7>" LOC = "G1"; # Bank = 3, Signal name = LD7
#NET "Led<6>" LOC = "P4"; # Bank = 2, Signal name = LD6
NET "Led<5>" LOC = "N4"; # Bank = 2, Signal name = LD5
NET "Led<4>" LOC = "N5"; # Bank = 2, Signal name = LD4
NET "Led<3>" LOC = "P6"; # Bank = 2, Signal name = LD3
NET "Led<2>" LOC = "P7"; # Bank = 3, Signal name = LD2
NET "Led<1>" LOC = "M11"; # Bank = 2, Signal name = LD1
NET "Led0" LOC = "M5"; # Bank = 2, Signal name = LD0
# Pin assignment for SWs
#NET "sw7" LOC = "N3"; # Bank = 2, Signal name = SW7
#NET "sw6" LOC = "E2"; # Bank = 3, Signal name = SW6
#NET "sw5" LOC = "F3"; # Bank = 3, Signal name = SW5
#NET "sw4" LOC = "G3"; # Bank = 3, Signal name = SW4
#NET "sw3" LOC = "B4"; # Bank = 3, Signal name = SW3
#NET "sw2" LOC = "K3"; # Bank = 3, Signal name = SW2
#NET "sw1" LOC = "L3"; # Bank = 3, Signal name = SW1
NET "sw0" LOC = "P11"; # Bank = 2, Signal name = SW0
#NET "btn3" LOC = "A7"; # Bank = 1, Signal name = BTN3
#NET "btn2" LOC = "M4"; # Bank = 0, Signal name = BTN2
#NET "btn1" LOC = "C11"; # Bank = 2, Signal name = BTN1
#NET "btn0" LOC = "G12"; # Bank = 0, Signal name = BTN0
## Pin assignment for PS2
#NET "ps2c" LOC = "B1" | DRIVE = 2 | PULLUP; # Bank = 3, Signal name = PS2C
#NET "ps2d" LOC = "C3" | DRIVE = 2 | PULLUP; # Bank = 3, Signal name = PS2D
```

Ůkol byl naprogramovat mealyho automat. Jedná se o výtah s 3 patry Je možné přepínat mezi těmito patry a aktualní patro se ukáže na sedmisegmentu Pokud zmáčkneme číslo patra ve kterém se výtah aktuálně náchází rozsvíti se příslušné 3 ledky.

Při práci s ISE project nastály 2 problémy z simulací. 1 problém byl v typu simulace změně typu z ModelSim na ISIM simulace fungovala. Dále mi nastala chyba při spuštění simulace mi antivirus zaznamená chybu a vypne mi simulaci, tento problém jsem vyřešil vypnutím antiviru.

Mimo tyto zmíněné problémy nenastaly žádné další nepříjemnosti.