

1.

Navrhněte Mealyho automat, který řeší otevírání skříňky na vlakovém nádraží. Cena je 5Kč, vhazované mince jsou 1,2 a 5-koruna. Automat vrátí 1Kč pouze v případě, že zákazník vhodil 4Kč a následně 2-korunovou minci.

2.

Spartan

Spartan je lehká vývojová deska FGA, je založena na řadě Xilinx Spartan-7. Můžete použít s Arduinem k ovládání LCD a fotoaparátu nebo jako samostatnou vývojovou desku FPGA.

Místo makrobuňek obsahují logické bloky

Log. Bloky jsou navzájem propojeny globální propojovací maticí

Obsahuje SRAM

VHDL

Používá se pro návrh a simulaci digitálních integrovaných obvodů, například programovatelných hradlových polí (CPLD, FPGA) nebo různých zákaznických obvodů (ASIC)

Jazyk VHDL může být použit i jako paralelní programovací jazyk.

3.

vstupní stavy			
	1 Kč	2 Kč	5 Kč
x0	0	0	0
x1	1	0	0
x2	0	1	0
x3	0	0	1

vnitřní stavy				
	Q1	Q2	Q3	
S0	0	0	0	...0 korun
S1	0	0	1	...1 koruna
S2	0	1	0	...2 koruny
S3	0	1	1	...3 koruny
s4	1	0	0	...4 koruny


výstupní stavy		
	otevřít	vrátit
y0	0	0
y1	1	0
y2	1	1

4.

$y = f(S)$ Moore... Závislý na vnitřním stavu

$y = f(X, S)$ Mealy... Závislý na vnitřním stavu a vstupu

5.

 

6.

	x0/y	x1/y	x2/y	x3/y
s0	s0/y0	s1/y0	s2/y0	s1/y0
s1	s1/y0	s2/y0	s3/y0	s1/y0
s2	s2/y0	s3/y0	s4/y0	s1/y0
s3	s3/y0	s4/y0	s0/y1	s1/y0
s4	s4/y0	s0/y1	s0/y2	s1/y0

7.

Dekoder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity dekoder is
    Port (
        HEX: in  STD_LOGIC_VECTOR (2 downto 0);
        LED: out STD_LOGIC_VECTOR (6 downto 0)
    );
end dekoder;

architecture Behavioral of dekoder is

begin

    with HEX select
    LED<= "1111001" when "001",    --1
        "0100100" when "010",    --2
        "0110000" when "011",    --3
        "0011001" when "100",    --4
        "0010010" when "101",    --5
        "1000000" when others; --0

end Behavioral;
  
```

Delicka

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity delicka is
    Port ( CLK_in : in  STD_LOGIC;
          CLK_out : out STD_LOGIC);
end delicka;

architecture Behavioral of delicka is

begin

    process (CLK_in)
        variable i : integer range 0 to 15000000 ;
    begin
        if rising_edge(CLK_in) then
            if i=0 then CLK_out <= '1' ;
                i := 9843000 ;
            else
                CLK_out <= '0' ;
                i := i - 1 ;
            end if ;
        end if ;
    end process;

end Behavioral;
```

Hlavní program

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity main is
    Port ( clock : in  STD_LOGIC;
          reset : in  STD_LOGIC;
          mince : in  STD_LOGIC_VECTOR (2 downto 0);
          otevrit : out STD_LOGIC_VECTOR (1 downto 0);
          stav : inout STD_LOGIC_VECTOR (2 downto 0));
end main;

architecture Behavioral of main is

    signal state, next_state : std_logic_vector(2 downto 0);

    constant s0 : std_logic_vector(2 downto 0) := "000";
    constant s1 : std_logic_vector(2 downto 0) := "001";
    constant s2 : std_logic_vector(2 downto 0) := "010";
    constant s3 : std_logic_vector(2 downto 0) := "011";
    constant s4 : std_logic_vector(2 downto 0) := "100";

begin

    SYNC_PROC: process (clock)
    begin

        if rising_edge (clock)
            then if (reset='0')
                then state <= next_state;
                else state <= s0;
                end if;
            end if;
        end process SYNC_PROC;
```

```

    OUTPUT_DECODE: process (mince,state)
Begin
case (state) is
    when s0 =>
        if (mince = "000") then otevrit <= "00";
        elsif (mince = "100") then otevrit <= "00";
        elsif (mince = "010") then otevrit <= "00";
        elsif (mince = "001") then otevrit <= "10";
        else otevrit <= "00";
        end if;
    when s1 =>
        if (mince = "000") then otevrit <= "00";
        elsif (mince = "100") then otevrit <= "00";
        elsif (mince = "010") then otevrit <= "00";
        elsif (mince = "001") then otevrit <= "10";
        else otevrit <= "00";
        end if;
    when s2 =>
        if (mince = "000") then otevrit <= "00";
        elsif (mince = "100") then otevrit <= "00";
        elsif (mince = "010") then otevrit <= "00";
        elsif (mince = "001") then otevrit <= "10";
        else otevrit <= "00";
        end if;
    when s3 =>
        if (mince = "000") then otevrit <= "00";
        elsif (mince = "100") then otevrit <= "00";
        elsif (mince = "010") then otevrit <= "10";
        elsif (mince = "001") then otevrit <= "10";
        else otevrit <= "00";
        end if;
    when s4 =>
        if (mince = "000") then otevrit <= "00";
        elsif (mince = "100") then otevrit <= "10";
        elsif (mince = "010") then otevrit <= "11";
        elsif (mince = "001") then otevrit <= "10";
        else otevrit <= "00";
        end if;

    when others => NULL;
end case;
stav <= state;
end process OUTPUT_DECODE;

NEXT_STATE_DECODE: process (state, mince)
begin
case (state) is
    when s0 =>
        if (mince = "000") then next_state <= s0; stav <="000";
        elsif (mince = "100") then next_state <= s1; stav <="001";
        elsif (mince = "010") then next_state <= s2; stav <="010";
        elsif (mince = "001") then next_state <= s0; stav <="000";
        else next_state <= s0;
        end if;

```

```

when s1 =>
    if (mince = "000") then next_state <= s1; stav <="001";
    elsif (mince = "100") then next_state <= s2; stav <="010";
    elsif (mince = "010") then next_state <= s3; stav <="011";
    elsif (mince = "001") then next_state <= s0; stav <="000";
    else next_state <= s1;
    end if;

when s2 =>
    if (mince = "000") then next_state <= s2; stav <="010";
    elsif (mince = "100") then next_state <= s3; stav <="011";
    elsif (mince = "010") then next_state <= s4; stav <="100";
    elsif (mince = "001") then next_state <= s0; stav <="000";
    else next_state <= s2;
    end if;

when s3 =>
    if (mince = "000") then next_state <= s3; stav <="011";
    elsif (mince = "100") then next_state <= s4; stav <="100";
    elsif (mince = "010") then next_state <= s0; stav <="000";
    elsif (mince = "001") then next_state <= s0; stav <="000";
    else next_state <= s3;
    end if;

when s4 =>
    if (mince = "000") then next_state <= s4; stav <="100";
    elsif (mince = "100") then next_state <= s0; stav <="000";
    elsif (mince = "010") then next_state <= s0; stav <="000";
    elsif (mince = "001") then next_state <= s0; stav <="000";
    else next_state <= s4;
    end if;


when others => NULL;
end case;
stav <= state;

end process NEXT_STATE_DECODE;

end Behavioral;


```

8.

 

Simulaci se mi nepodařilo udělat čitelnější tak jsem jí poslal s protokolem

9.

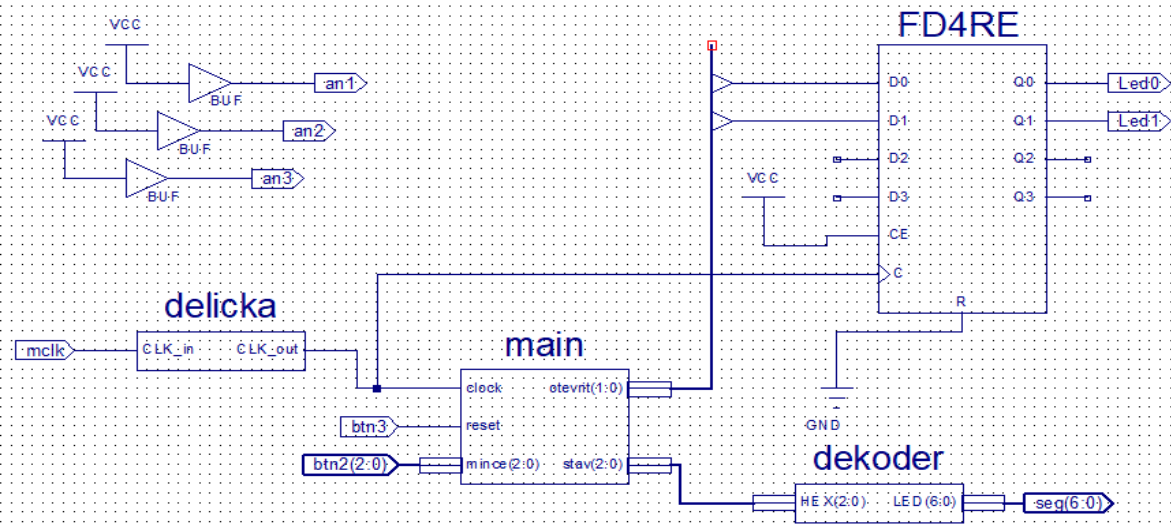

10.

clock pins for Basys2 Board

NET "mclk" LOC = "B8"; # Bank = 0, Signal name = MCLK

Pin assignment for DispCtl

Connected to Basys2 onBoard 7seg display

NET "seg<0>" LOC = "L14"; # Bank = 1, Signal name = CA

NET "seg<1>" LOC = "H12"; # Bank = 1, Signal name = CB

NET "seg<2>" LOC = "N14"; # Bank = 1, Signal name = CC

NET "seg<3>" LOC = "N11"; # Bank = 2, Signal name = CD

NET "seg<4>" LOC = "P12"; # Bank = 2, Signal name = CE

NET "seg<5>" LOC = "L13"; # Bank = 1, Signal name = CF

NET "seg<6>" LOC = "M12"; # Bank = 1, Signal name = CG

#NET "dp" LOC = "N13"; # Bank = 1, Signal name = DP

NET "an3" LOC = "K14"; # Bank = 1, Signal name = AN3

NET "an2" LOC = "M13"; # Bank = 1, Signal name = AN2

NET "an1" LOC = "J12"; # Bank = 1, Signal name = AN1

#NET "an0" LOC = "F12"; # Bank = 1, Signal name = AN0

Pin assignment for LEDs

#NET "Led<7>" LOC = "G1"; # Bank = 3, Signal name = LD7

NET "Led<6>" LOC = "P4"; # Bank = 2, Signal name = LD6

NET "Led<5>" LOC = "N4"; # Bank = 2, Signal name = LD5

NET "Led<4>" LOC = "N5"; # Bank = 2, Signal name = LD4

NET "Led<3>" LOC = "P6"; # Bank = 2, Signal name = LD3

NET "Led<2>" LOC = "P7"; # Bank = 3, Signal name = LD2

NET "Led<1>" LOC = "M11"; # Bank = 2, Signal name = LD1

NET "Led0" LOC = "M5"; # Bank = 2, Signal name = LD0

Pin assignment for SWs

#NET "sw7" LOC = "N3"; # Bank = 2, Signal name = SW7

#NET "sw6" LOC = "E2"; # Bank = 3, Signal name = SW6

#NET "sw5" LOC = "F3"; # Bank = 3, Signal name = SW5

#NET "sw4" LOC = "G3"; # Bank = 3, Signal name = SW4

```
#NET "sw3" LOC = "B4"; # Bank = 3, Signal name = SW3
#NET "sw2" LOC = "K3"; # Bank = 3, Signal name = SW2
#NET "sw1" LOC = "L3"; # Bank = 3, Signal name = SW1
NET "sw0" LOC = "P11"; # Bank = 2, Signal name = SW0
```

```
NET "btn3" LOC = "A7"; # Bank = 1, Signal name = BTN3
NET "btn2" LOC = "M4"; # Bank = 0, Signal name = BTN2
NET "btn1" LOC = "C11"; # Bank = 2, Signal name = BTN1
NET "btn0" LOC = "G12"; # Bank = 0, Signal name = BTN0
```

Pin assignment for PS2

```
#NET "ps2c" LOC = "B1" | DRIVE = 2 | PULLUP ; # Bank = 3, Signal name = PS2C
#NET "ps2d" LOC = "C3" | DRIVE = 2 | PULLUP ; # Bank = 3, Signal name = PS2D
```

11.

Úkol byl naprogramovat mealyho automat.

Jedná se o skříňku

pro zaplacení lístku je nutné zaplatit 5 korun

Je možné vhadzovat 1,2 a 5 korun, celkový počet se pak následně ukáže na sedmisegmentu

Dále byla podmínka že pokud je ve skříňce 4 koruny a vložíme další 2 automat nám vrátí 1 korunu.

v jiných případech automat nevrací nic

Při práci s ISE project nastály 2 problémy z simulací.

1 problém byl v typu simulace změně typu z ModelSim na ISIM simulace fungovala.

Dále mi nastala chyba při spuštění simulace mi antivirus zaznamená chybu,vypne mi simulaci, tento problém jsem vyřešil vypnutím antiviru.

Mimo tyto zmíněné problémy nenastaly žádné další nepříjemnosti.